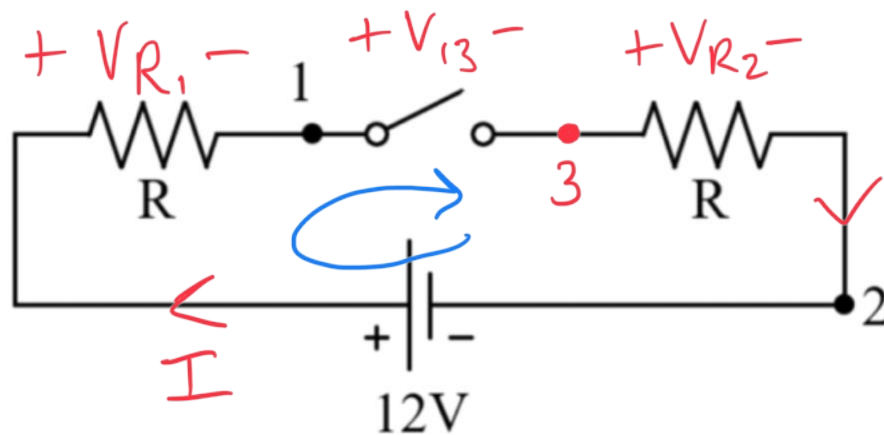


MAE 3780/3783: Mechatronics
January 29, 2024

Logistics Updates

- This week in lab – **Lab 1**
 - Tinkercad prelab 15 minutes before lab session
 - Written prelab printed or shown on device at beginning of lab section
- HW 2 (resistors) released on asap – Due **Friday, February 9, 11 pm**
- Fill out when2meet with availability/OH preferences



What is the voltage difference between points 1 and 2?

☐ 0V

☐ 6V

☒ 12V

$$V_{32} = V_{R2} = 0$$

$$V_{12} = V_{13} + V_{32} \rightarrow 0$$

$$V_{12} = V_{13} = 12V$$

From KVL:

$$-12 + V_{R1} + V_{13} + V_{R2} = 0$$

From KCL:

$$I = 0$$


From Ohm's Law:

$$V_{R1} = R \cdot I = 0$$

$$V_{R2} = R \cdot I = 0$$


$$-12 + 0 + V_{13} + 0 = 0$$

$$V_{13} = 12V$$

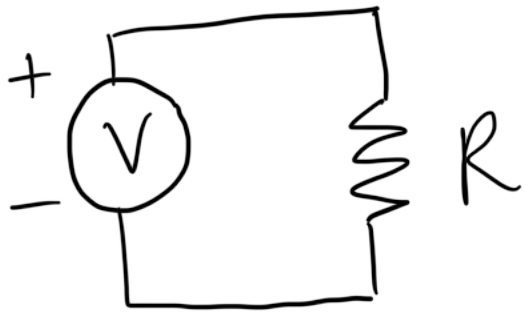

$$R \rightarrow \infty$$

$$I = \frac{V}{R} = 0$$

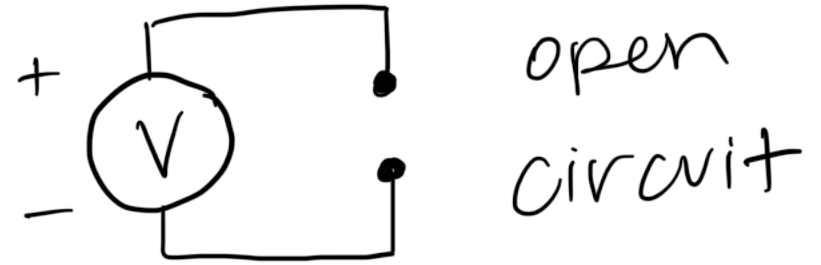

there is no complete path for current to flow






$$R \rightarrow 0$$

$$I = \frac{V}{R} \rightarrow \infty$$




* can result in dangerously high currents/melting things

Practical Sources

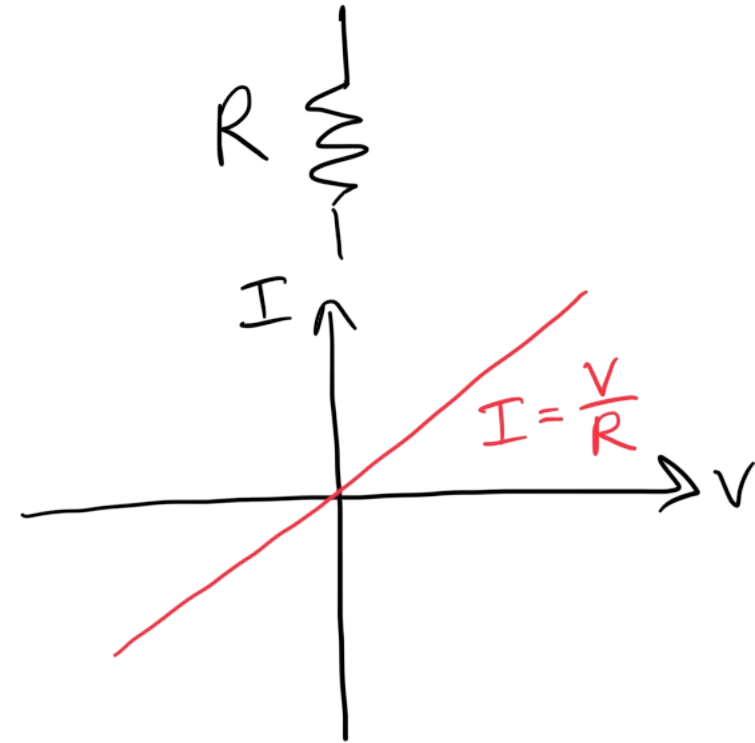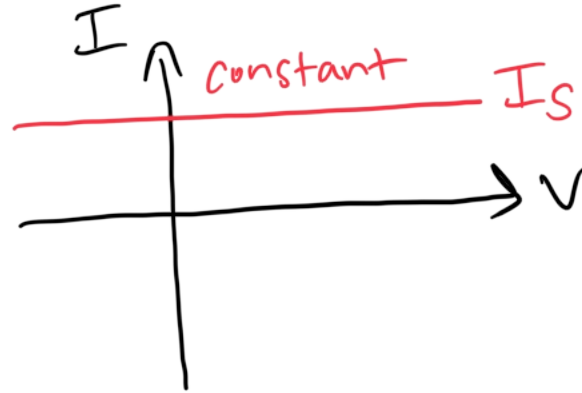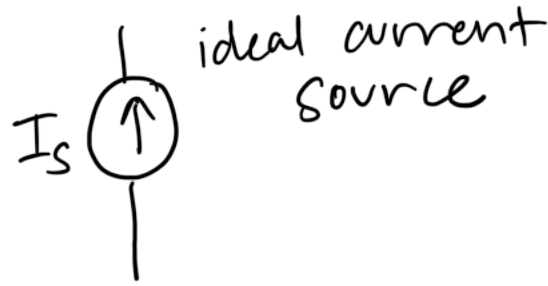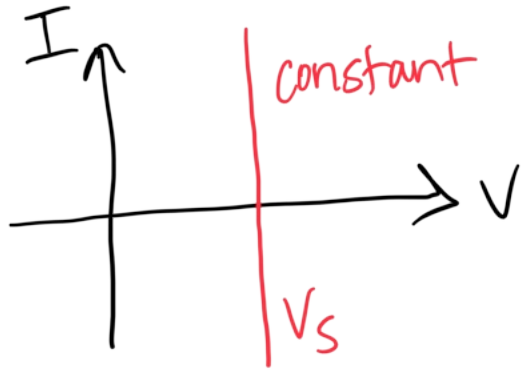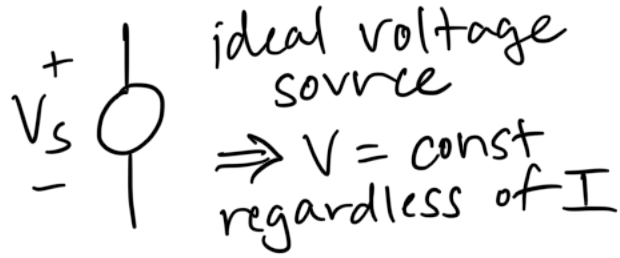

Ideally :

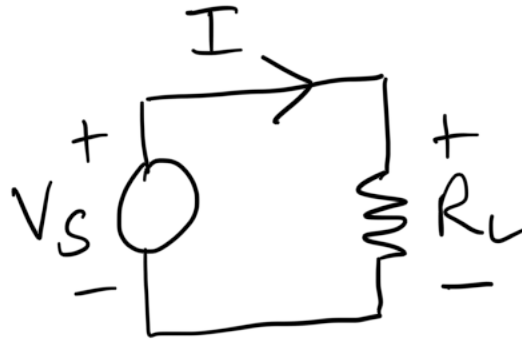


$$V = R \cdot I$$

$$\text{as } R_L \rightarrow 0, I \rightarrow \infty$$

practically, I is bounded

modeled as:

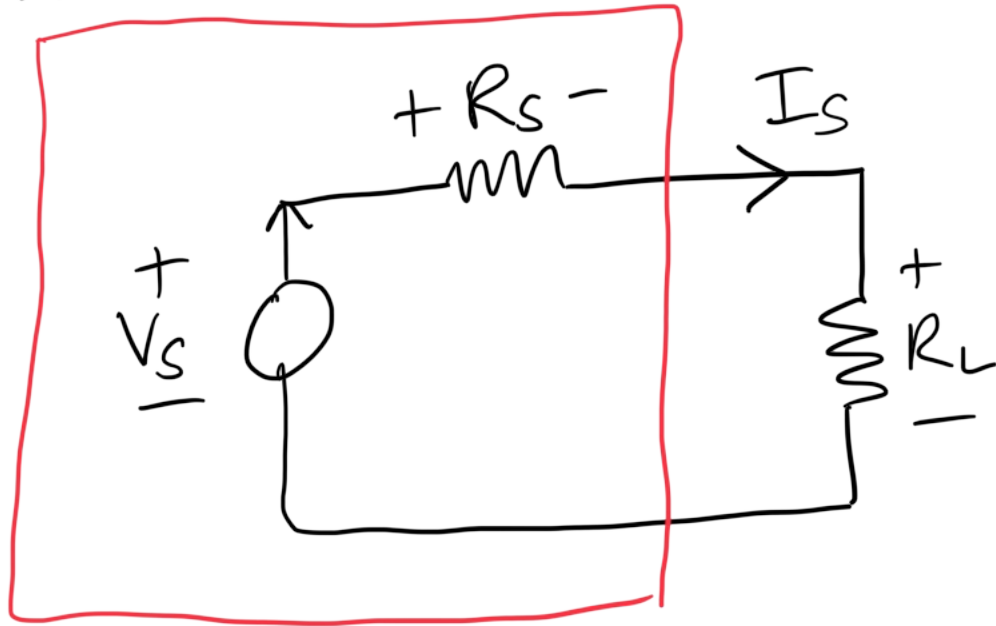

voltage source

effect on R_L :


$$V_{R_L} = I_s \cdot R_L = \frac{V_s}{R_s + R_L} \cdot R_L = V_s \frac{R_L}{R_s + R_L}$$

want R_s to be small

if $R_L = 0$,
max current

$$I_{s\max} = \frac{V_s}{R_s}$$


similarly for current sources,

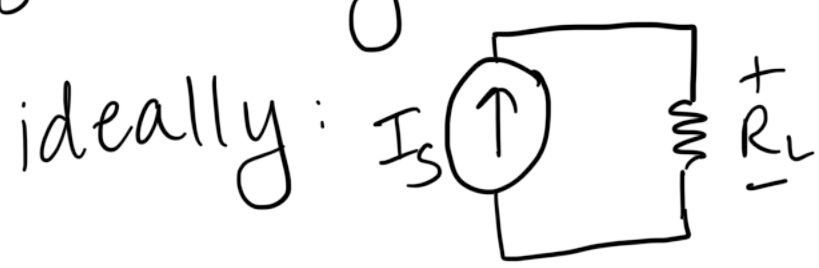


$$I = \frac{V}{R}$$

as $R \rightarrow \infty$, $V \rightarrow \infty$


practically, V is bounded (R_s)

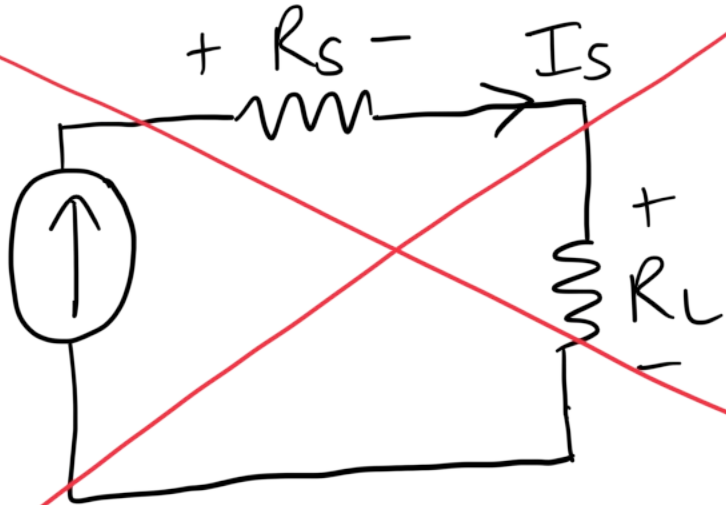

\equiv

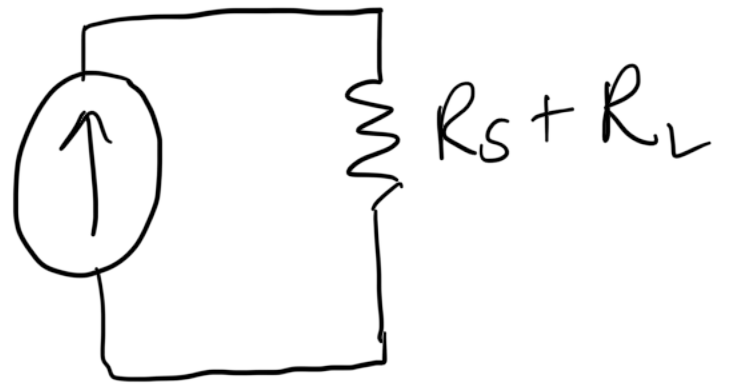

$$I_s = \frac{V}{R_s + R_L}$$

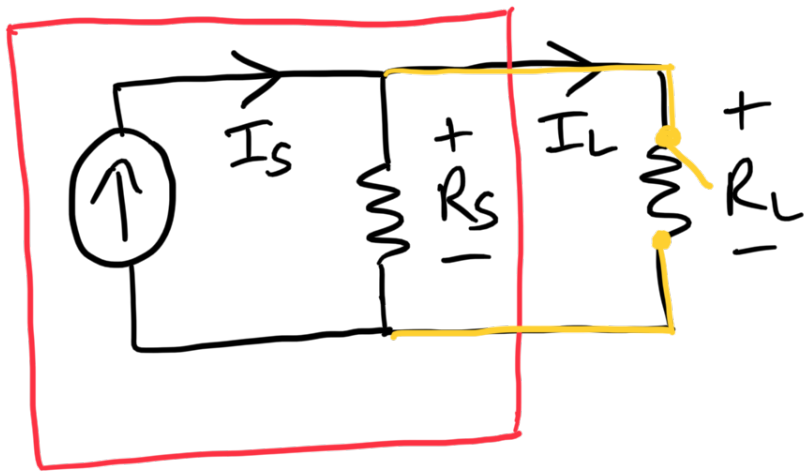

$$V_{L\max} = I_s R_s$$

as $R_L \rightarrow \infty$,

open circuit

current source

effect on R_L :

$$I_L = I_s - \frac{V_L}{R_s}$$

want R_s to be large