

MAE 3780/3783: Mechatronics
January 31, 2024

Logistics Updates


- This week in lab – **Lab 1**
 - Tinkercad prelab 15 minutes before lab session
 - Written prelab printed or shown on device at beginning of lab section
 - Set dial to 10A jack, make sure it's safe, and then move on to the 200mA jack
- 3. Measure the current through the LED.
 - a. Move the red probe to the "mA" jack.
 - b. Set the dial to 200mA DC (the "A" with straight and dashed lines next to it).
- HW 2 (resistors) was released at 10 am
 - Due **Friday, February 9, 11 pm**
- Reminder: Email formatting & contents

Measurement Devices

Voltmeter: connected in parallel
 \Rightarrow "should not" draw current


Ammeter: connected in series
 \Rightarrow "should not" have a voltage drop

practically,

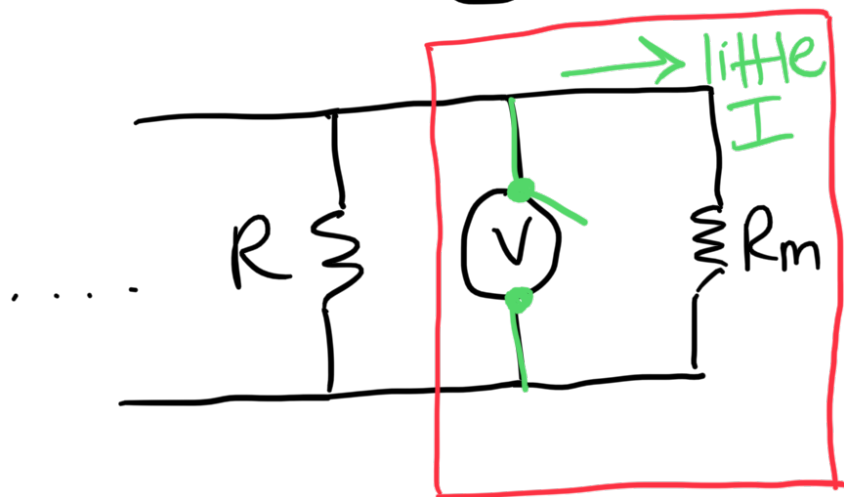

voltmeter

want R_m to be
large

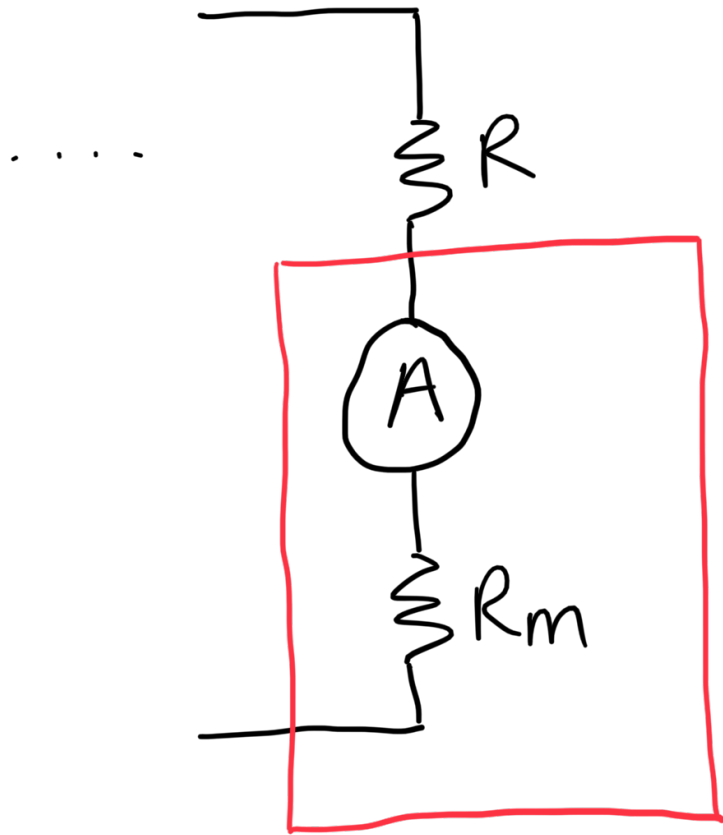

ammeter

want R_m to be
small

Circuit Analysis

find I, V for all devices


- Req (KVL, KCL, Ohm's Law)

- Node analysis


- Mesh analysis

} systematic way
of writing
equations
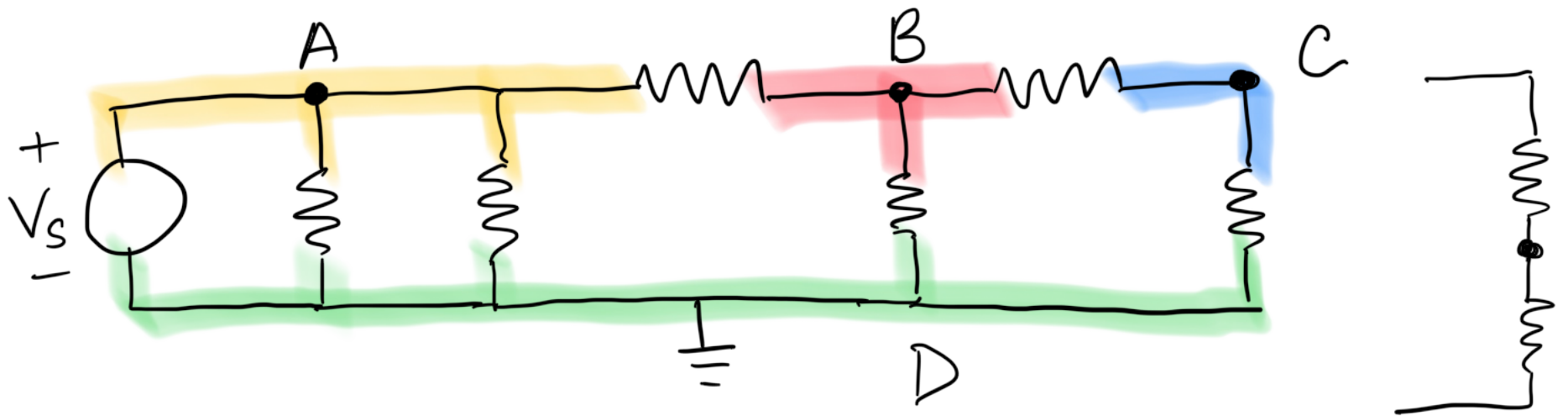
$$\begin{array}{ccccc} A & X & = & b & \\ \uparrow & \uparrow & & \swarrow & \\ \text{known} & \text{unknown} & & \text{known} & \end{array}$$



Example:

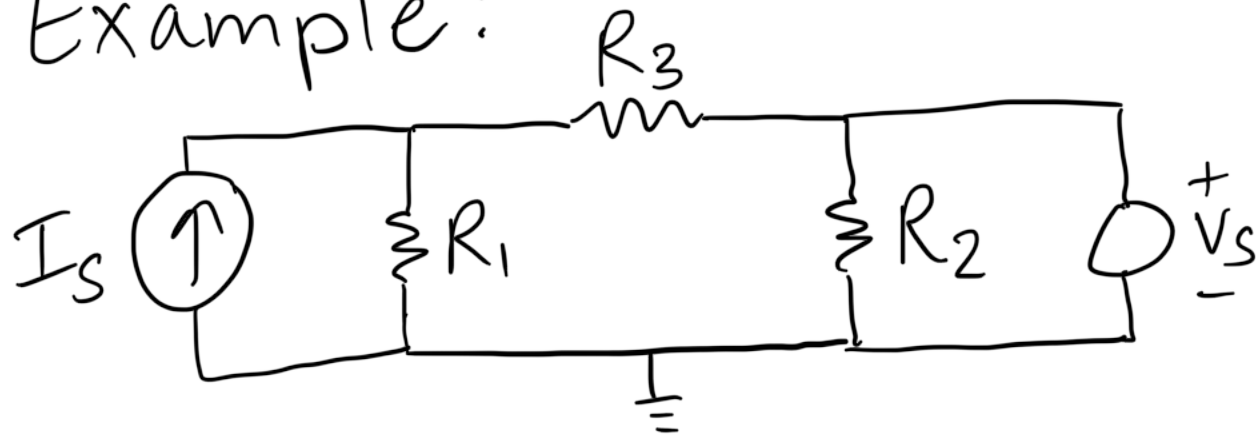

$$V_{R_3} = ?$$


Node analysis:

unknowns: ① voltages at nodes
② currents at voltage sources

Known: ① sources

equations to use:

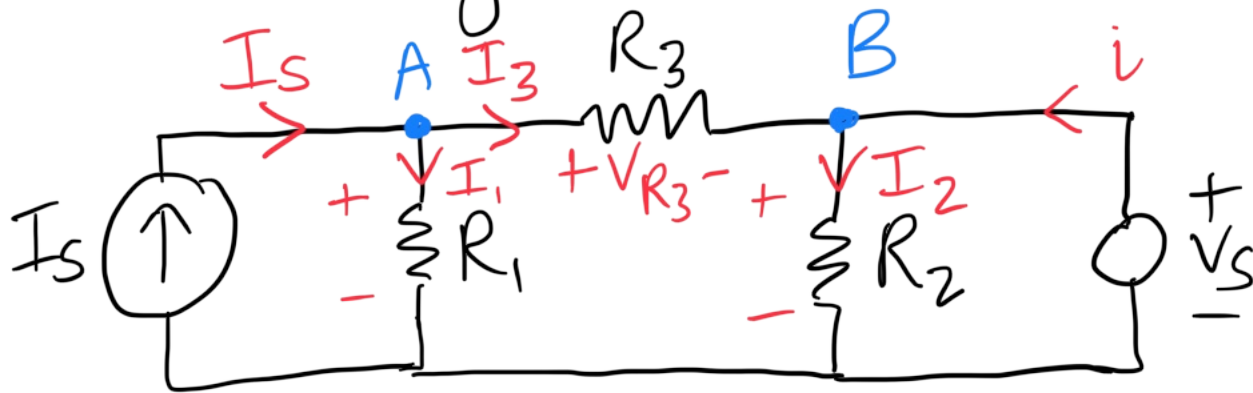- KCL represented using voltages
- voltage sources



unknowns: V_A , V_B , i

KCL at nodes:

node A: $I_s = I_1 + I_3$

ohm's law: $I_s = \frac{1}{R_1} V_A + \frac{1}{R_3} (V_A - V_B)$

$$\left(\frac{1}{R_1} + \frac{1}{R_3}\right) V_A - \frac{1}{R_3} V_B = I_s \quad \text{Known}$$

node B: $I_3 + i = I_2$

ohm's law: $\frac{1}{R_3} (V_A - V_B) + i = \frac{1}{R_2} V_B$

$\frac{1}{R_3} V_A - \left(\frac{1}{R_3} + \frac{1}{R_2}\right) V_B + i = 0$ known

voltage source: $V_S = V_B$

together:

$$\begin{bmatrix} \frac{1}{R_1} + \frac{1}{R_3} & -\frac{1}{R_3} & 0 \\ \frac{1}{R_3} & -\left(\frac{1}{R_3} + \frac{1}{R_2}\right) & 1 \\ 0 & 1 & 0 \end{bmatrix} \begin{bmatrix} V_A \\ V_B \\ i \end{bmatrix} = \begin{bmatrix} I_S \\ 0 \\ V_S \end{bmatrix}$$

A X b

originally incorrectly written
in lecture; this is correct

$$Ax = b \implies x = A^{-1}b$$